

Template Week 2 – Logic

Student number: 593201

Assignment 2.1: Parking lot

Which gates do you need?

- A 3-input AND gate will output 1 (FULL) only when Parking lot 1, 2, and 3 are all 1.
- This matches the requirement that the sign lights up only when all spaces are occupied.

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Assignment 2.2: Android or iPhone

Which gates do you need?

You need an XOR (Exclusive OR) gate.

- An XOR gate outputs 1 only when one input is 1 and the other is 0.
- If both are 0 (no phone chosen) or both are 1 (both phones chosen), the output is 0.

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

Assignment 2.3: Four NAND gates

Complete this table

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

How can the design be simplified?

- The current design uses four NAND gates to implement the logic.
- Since the resulting behavior is XOR, the circuit can be simplified by:
 - Replacing the four NAND gates with one XOR gate, or
 - Using fewer gates if XOR is available as a standard logic component.


Conclusion:

- The four-NAND-gate circuit is a NAND-only implementation of an XOR gate.
- Using a single XOR gate would make the circuit simpler, smaller, and more efficient.

Assignment 2.4: Getting to know Logisim evolution


Screenshot of the design with your name and student number in it:

Dylan Holkenborg 593201

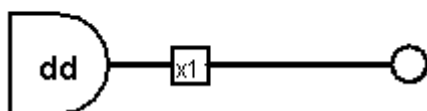


Assignment 2.5: SR Latch

Screenshot SR Latch in Logisim with your name and student number:

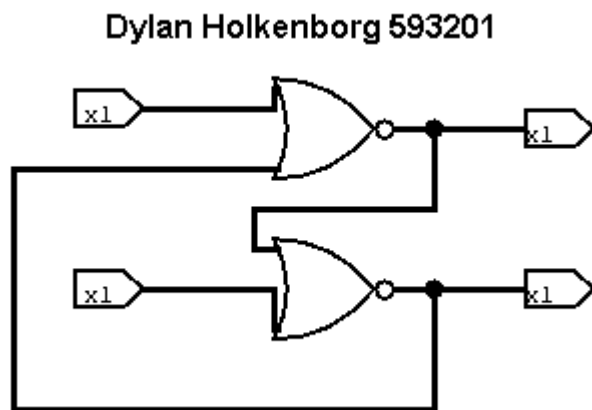

Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:

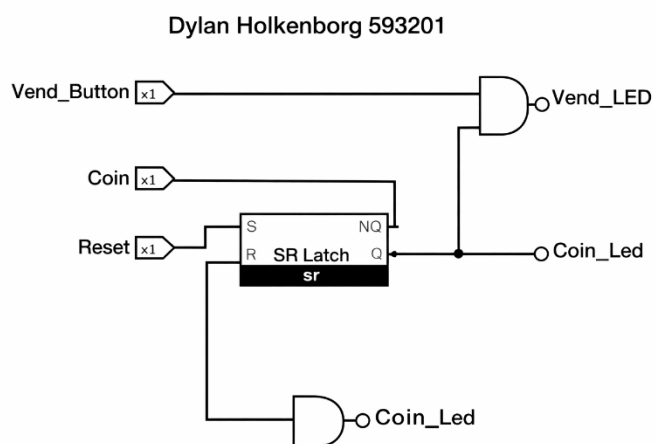

Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

```
public class Main {  
    public static void main(String[] args) {  
        int number = 6;  
  
        if ((number & 1) == 1) System.out.println("number is odd");  
        else System.out.println("number is even");  
    }  
}
```

Assignment 2.8: Java Application Bit Calculations

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

Paste source code here, with a screenshot of a working application.

```
Menu:
1) Is number odd?
2) Is number a power of 2?
3) Two's complement of number?
0) Exit
Choose option: 0
Bye!

Process finished with exit code 0
```

```
public class Main {
    public static void main(String[] args) throws Exception {
        int number = readInt("Enter an integer: ");
        while (true) {
            printMenu();
            int option = readInt("Choose option: ");
            if (option == 0) {
                System.out.println("Bye!");
                break;
            }
            switch (option) {
                case 1:
                    System.out.println("Result: " + number + (isOdd(number) ? " is odd" : " is even"));
                    break;
                case 2:
                    System.out.println("Result: " + number + (isPowerOfTwo(number) ? " IS" : " is NOT") + " a power
of 2");
                    break;
                case 3:
                    System.out.println("Result: two's complement (bitwise) = " + twosComplement(number));
                    break;
                default:
                    System.out.println("Invalid option. Choose 0-3.");
                    break;
            }
        }
    }
}
```

```
private static void printMenu() {
    System.out.println();
    System.out.println("Menu:");
    System.out.println("1) Is number odd?");
    System.out.println("2) Is number a power of 2?");
    System.out.println("3) Two's complement of number?");
    System.out.println("0) Exit");
}

// Reads an integer from stdin (no Scanner).
private static int readInt(String prompt) throws Exception {
    while (true) {
        System.out.print(prompt);
        String line = readLine();
```

```

    line = trim(line);
    if (line.length() == 0) continue;
    boolean negative = false;
    int i = 0;
    if (line.charAt(0) == '-') {
        negative = true;
        i = 1;
        if (line.length() == 1) continue;
    }
    int value = 0;
    boolean ok = true;
    while (i < line.length()) {
        char c = line.charAt(i);
        if (c < '0' || c > '9') {
            ok = false;
            break;
        }
        int digit = c - '0';
        // basic overflow-safe build (still fine for normal inputs)
        value = value * 10 + digit;
        i++;
    }
    if (!ok) {
        System.out.println("Please enter a valid integer.");
        continue;
    }
    return negative ? -value : value;
}
}

// Reads a line from System.in using System.in.read().
private static String readLine() throws Exception {
    StringBuilder sb = new StringBuilder();
    int ch;
    while ((ch = System.in.read()) != -1) {
        if (ch == '\r') continue;
        if (ch == '\n') break;
        sb.append((char) ch);
    }
    return sb.toString();
}

// Trim spaces/tabs without using imports
private static String trim(String s) {
    int start = 0;
    int end = s.length() - 1;
    while (start <= end && isWhitespace(s.charAt(start))) start++;
    while (end >= start && isWhitespace(s.charAt(end))) end--;
    if (start > end) return "";
    return s.substring(start, end + 1);
}

```

```

}
private static boolean isWhitespace(char c) {
    return c == ' ' || c == '\t';
}
// 1) Odd if LSB is 1
private static boolean isOdd(int n) {
    return (n & 1) != 0;
}
// 2) Power of 2: n > 0 and only one bit set
private static boolean isPowerOfTwo(int n) {
    return n > 0 && (n & (n - 1)) == 0;
}
// 3) Two's complement using bitwise ops: ~n + 1
private static int twosComplement(int n) {
    return (~n) + 1;
}
}

```

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)